



Faculty Of Engineering

The Hashemite University, Zarqa - Jordan April

2024

Computer Architecture

Bus Based Architecture

| <i>Student Name</i> | <i>ID#</i> |
|-------------------------|----------------|
| <i>Issa Qandah</i> | <i>2036177</i> |
| <i>Hassan TaqiEddin</i> | <i>2036057</i> |

Table of content :

| | |
|--|-----------|
| <i>Introduction</i> | <i>3</i> |
| <i>Components</i> | <i>5</i> |
| <i>Register File</i> | <i>5</i> |
| <i>Register File Schematic design</i> | <i>6</i> |
| <i>Register File Testing</i> | <i>7</i> |
| <i>ALU</i> | <i>11</i> |
| <i>ALU Operations</i> | <i>11</i> |
| <i>ALU Testing</i> | <i>12</i> |
| <i>ImmGen</i> | <i>15</i> |
| <i>ImmGen Testing</i> | <i>15</i> |
| <i>Memory</i> | <i>16</i> |
| <i>Memory Testing</i> | <i>17</i> |
| <i>Data path</i> | <i>20</i> |
| <i>Data path schematic design</i> | <i>20</i> |
| <i>Supported instructions and their microcodes</i> | <i>21</i> |
| <i>Datapath testing</i> | <i>24</i> |
| <i>Micro coded Control Unit</i> | <i>31</i> |

1. Introduction

In this phase we made the data path including all previous modules (RegisterFile,ALU) and made new modules (DataMemory,ImmGen,other registers, and muxes).

In bus-based architecture based on RISC-V ISA, which is an open-source, streamlined design for computer processors, emphasizing simplicity and adaptability. It uses a reduced instruction set computing (RISC) approach with a small set of basic instructions, making it efficient and flexible for a wide range of applications.

The bus is shared between all components, and it is defined as wire (with multiplexers to determine which read and which write) and only one of the shared components can write per cycle.

Microprogramming is applied here, which is a technique used in computer architecture where complex instructions of a CPU are broken down into simpler microinstructions stored in a control memory.

These microinstructions control the operations of the CPU's control unit, allowing for efficient execution of instructions.

By using microprogramming, CPUs can be designed more flexibly, enabling easier modification and optimization of instruction sets without altering the hardware design.

here which has these characteristics:

- *High CPI relatively:* as it involves additional overhead in fetching and executing microinstructions.
- *Cycle duration becomes small (Higher frequency):* allowing for more efficient instruction execution through finer control over hardware operations.
- *Easy to apply more instructions:* offering flexibility in expanding the range of supported operations without necessitating significant hardware modifications.

Until now there is no control unit implementation, so there is need to manually write the input signal to the datapath to make sure that the design is working properly, however control unit is going to be implemented at the next phase.

*One modification we made on the reference design is removing the (ALU Control) module replacing it with 4-bits **ALUOp** signal coming directly from the control unit.*

The design has 32-general purpose registers and another 4-special purpose registers (A,B,PC,IR), however PC register is placed inside the register file.

There is only one memory, that contains the instruction segment and the data segment and it has Busy signal which will be discussed in its section.


Immediate generation module has four types of immediate extension (I,S,B,J) each one has its use in term of type of extension (Zero or signed) and how many bits is extended.

2. Components

2.1 Register File:


| Component Description | |
|------------------------------|---|
| Registers | 32 General Purpose Registers (GPRs) + PC register |
| Address Input | 6-bit address (addr), determines which register is to be read or written to |
| Data Port | Bidirectional, 32-bit |
| Control Signals | RegWr: Determines read/write operation (1 for write, 0 for read) enReg: General enable control, If enReg is 1, then the register reads or writes depending on RegWr. If enReg is 0, then nothing is done |
| Read Operation | Asynchronous |
| Write Operation | On positive edge of clock |
| 64x1 Decoder | Decodes the 6-bit address input to select a specific register to write on |
| 64 by 6 Mux | Selects register output data to read from based on address input |
| Tri-state Buffer | 2 Tri-state Buffers, in case of reading from register file the write buffer puts the port on z state to allow the reading buffer putting data on the port, in case of writing on register file, the reading buffer puts the port on z state allowing the writing buffer to put data on the port |

2.1.1 Schematic design:

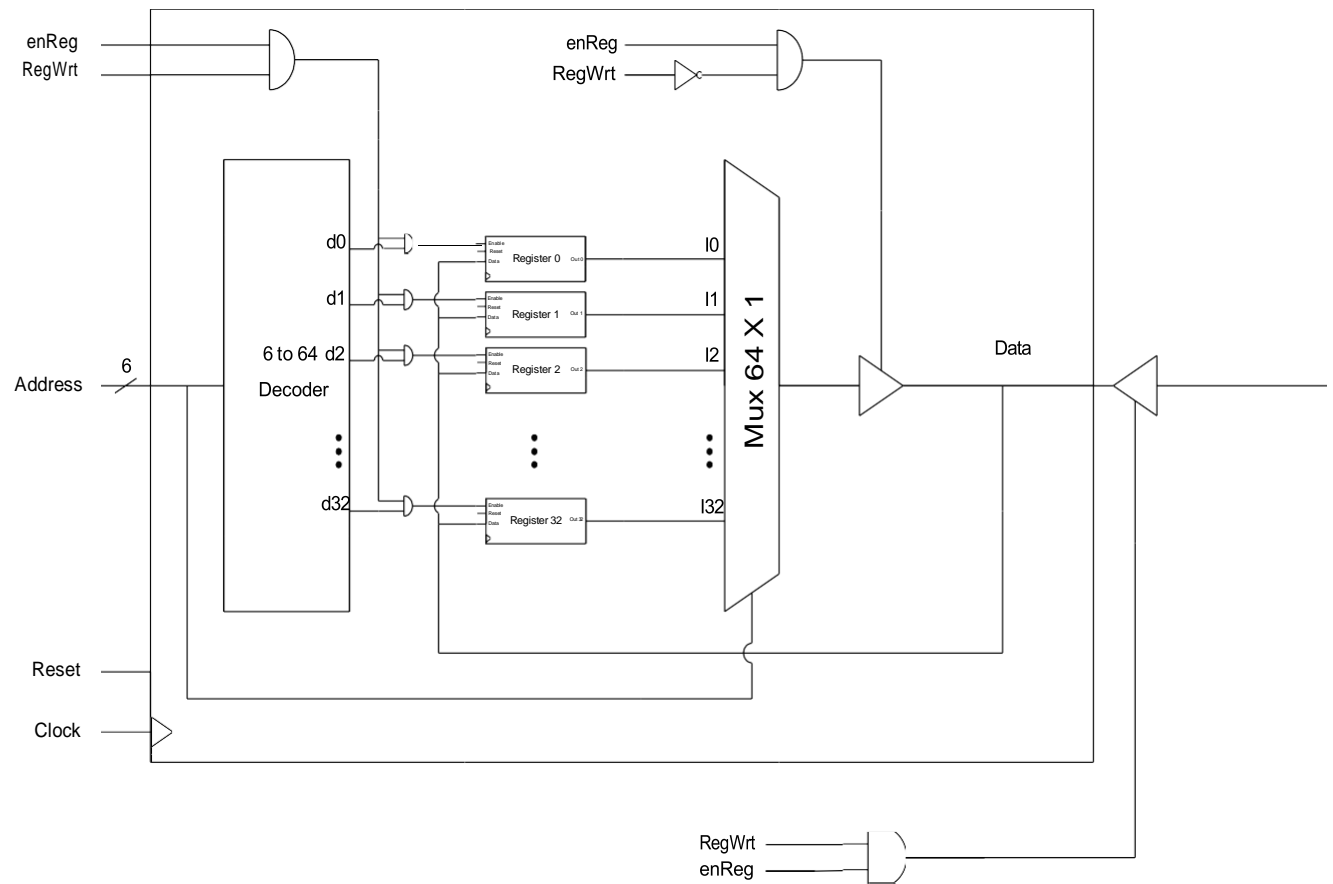

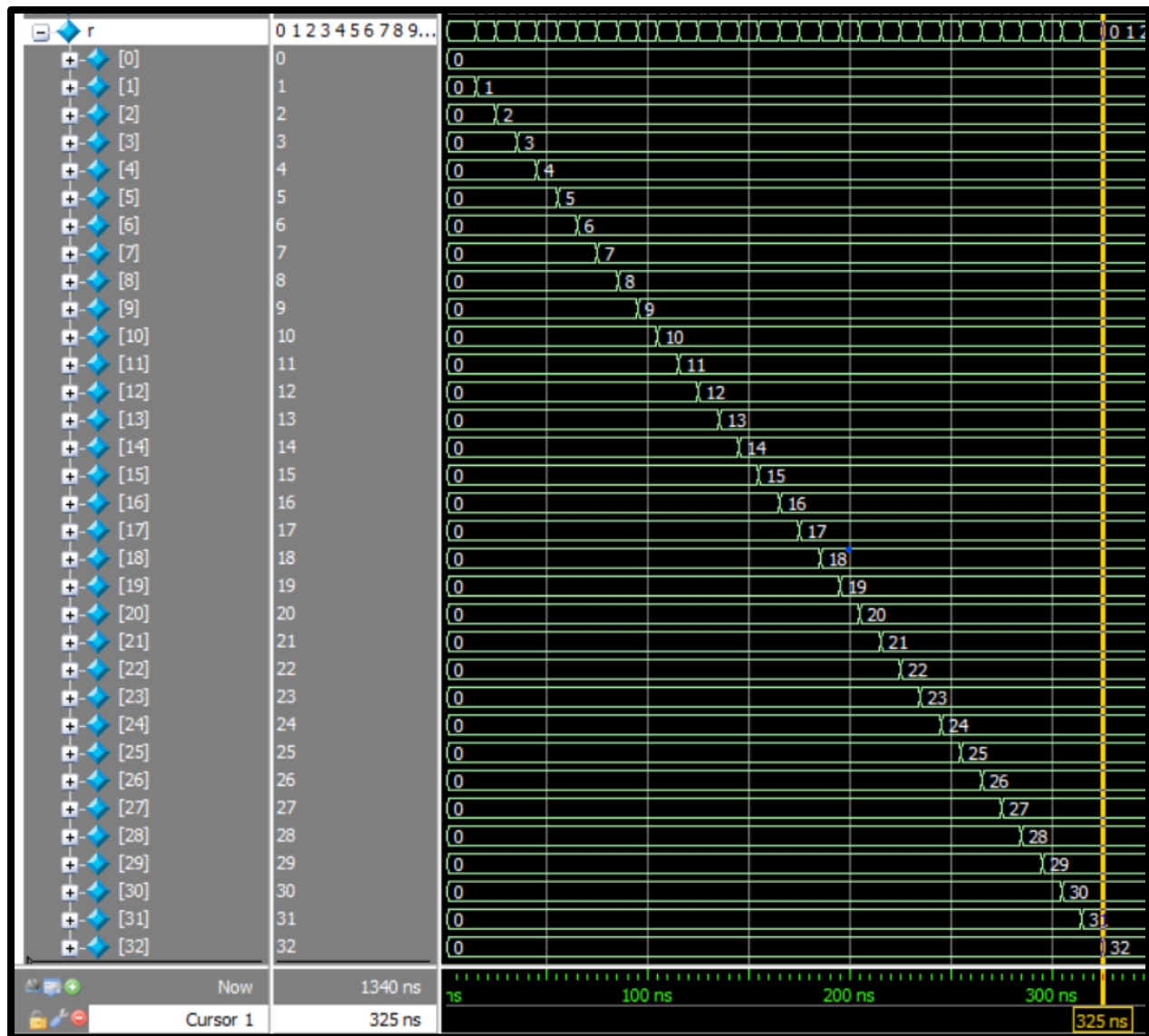
2.1.2 Register File Testing

Test case 1.1: Writing on all registers their addresses as values while “RegWrt, enReg” signals are enabled.





Test case 1.2: Read all register values in descending order after the write operation.

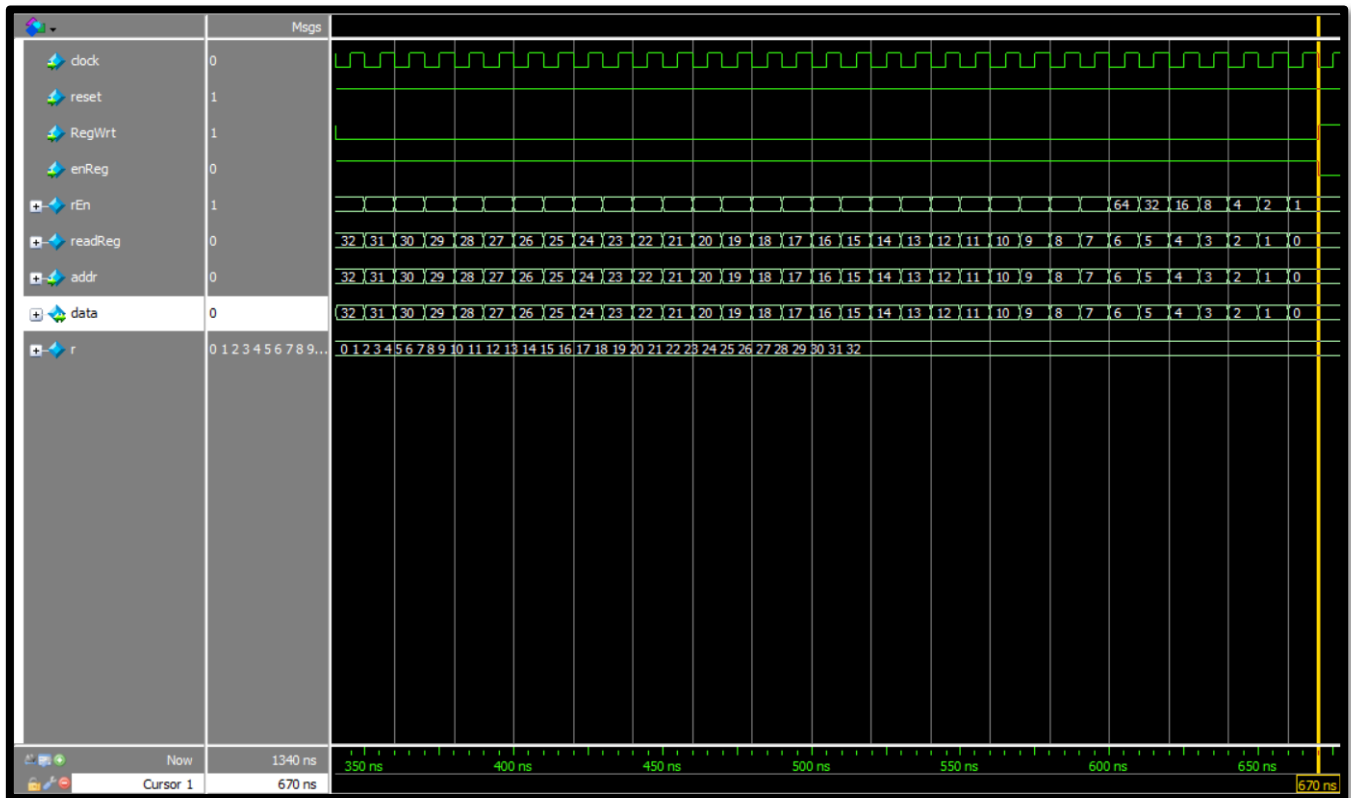Note the signals at first, then see addresses and data are the same values



 Test case 2.1: Attempt to write zero value on all registers with the "enReg" signal deactivated.
 No write operation occurs, and register values remain unchanged.



 

2.2 ALU

This ALU (Arithmetic and Logical Unit) performs 10-operations which is enough to implement the majority of RISC-V instructions, these operands are special purpose register (A, B), to make the ALU operation.

Here is our 10 operations and their needed operations (This table might be changed later)

| Operation | Alu Op | Mirco Operation |
|------------------|----------------|-------------------------|
| <i>COPY_A</i> | <i>4'b0000</i> | <i>A-> Bus</i> |
| <i>COPY_B</i> | <i>4'b0001</i> | <i>B -> Bus</i> |
| <i>INC_A_1</i> | <i>4'b0010</i> | <i>A+1 ->Bus</i> |
| <i>DEC_A_1</i> | <i>4'b0011</i> | <i>A-1 ->Bus</i> |
| <i>INC_A_4</i> | <i>4'b0100</i> | <i>A+4 -> Bus</i> |
| <i>DEC_A_4</i> | <i>4'b0101</i> | <i>A-4 -> Bus</i> |
| <i>ADD</i> | <i>4'b0110</i> | <i>A+B -> Bus</i> |
| <i>SUB</i> | <i>4'b0111</i> | <i>A-B -> Bus</i> |
| <i>AND</i> | <i>4'b1000</i> | <i>A&B ->Bus</i> |
| <i>OR</i> | <i>4'b1001</i> | <i>A B ->Bus</i> |

2.2.1 ALU Testing

Testing here is based on the opcode and each operation has been tested twice, first time to compute random values based on the inputs and opcode and the second time checking the zero flag along with testing its functionality.

Test case:

There are 3 test cases here:

Note: All zero-flag testing has the same expected output.

1: Testing COPY_A operation


Expected output: data = 0xffffffff, zero = 0

2: Testing COPY_B operation

Expected output: data = 0x0000ffff, zero = 0

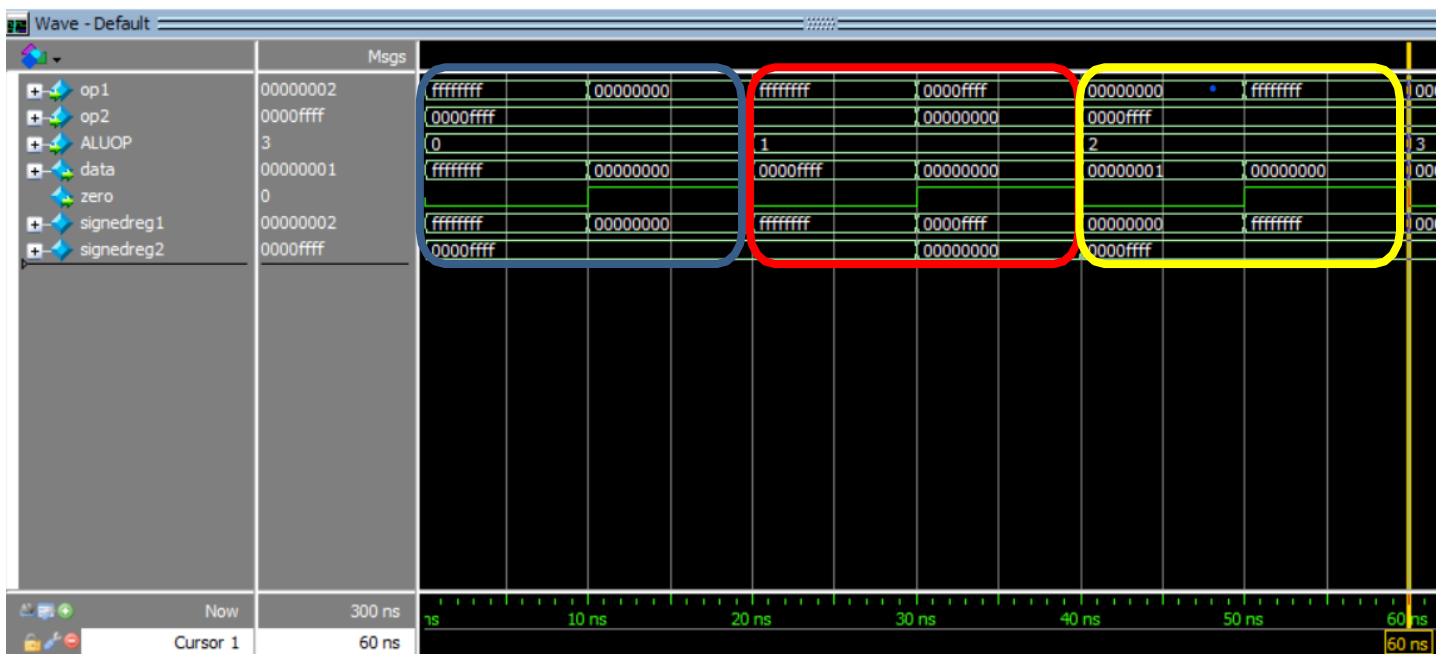3: Testing INC_A_1 operation

Expected output: data = 0x00000001, zero = 0



4: Testing DEC_A_1 operation


Expected output: data = 0x00000001, zero = 0

5: Testing INC_A_4 operation

Expected output: data = 0x00000004, zero = 0

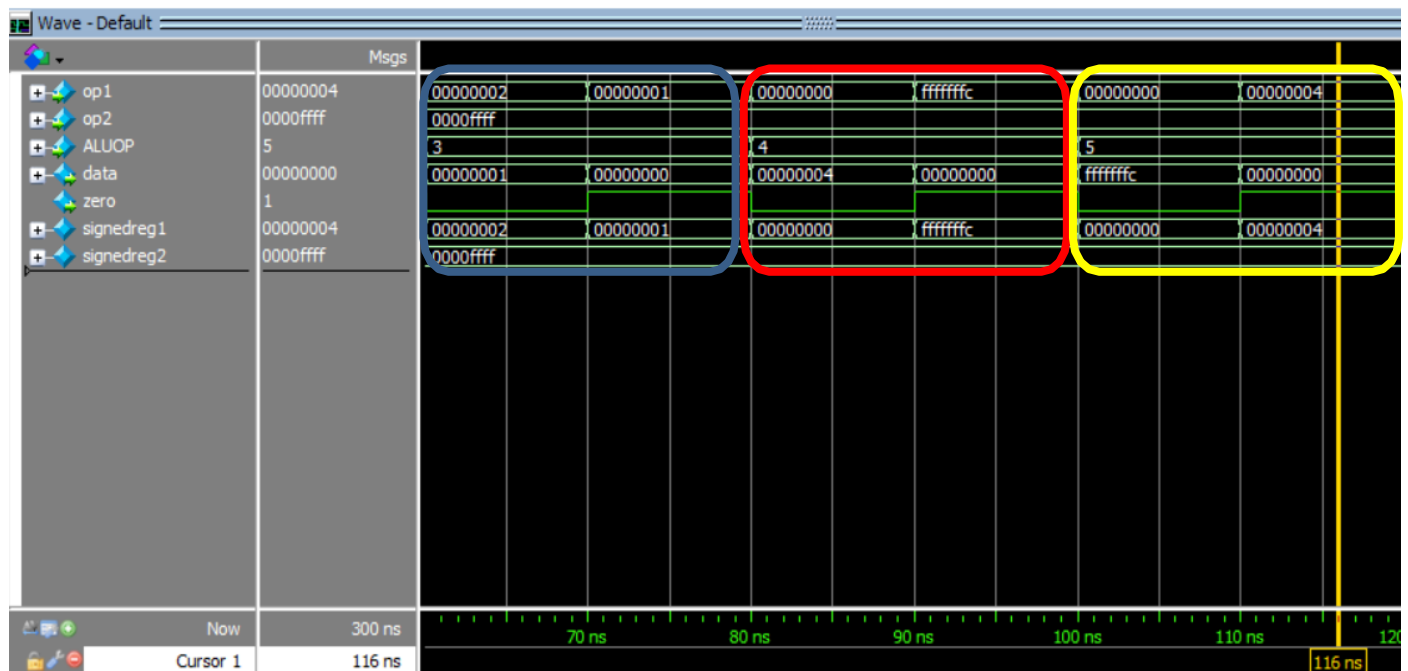6: Testing DEC_A_4 operation

Expected output: data = 0xffffffffc, zero = 0



7: Testing ADD operation

Expected output: data = 0xffffffff, zero = 0

8: Testing SUB operation


Expected output: data = 0xffffffff0, zero = 0

9: Testing AND operation

Expected output: data = 0xf000000c, zero = 0

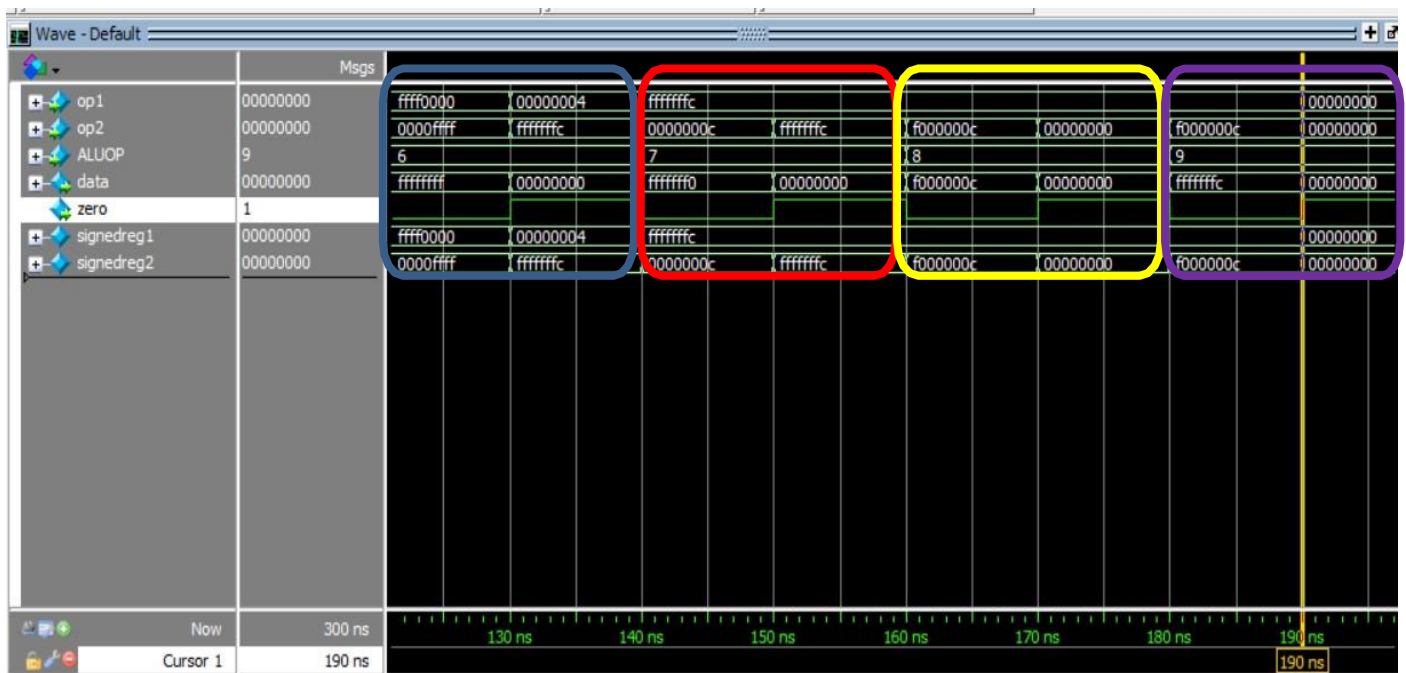10: Testing OR operation

Expected output: data = 0xffffffffc, zero = 0



2.3 ImmGen

This module has four types of immediate extension (I,S,B,J) each one has its use in term of type of extension (Zero or signed) and how many bits is extended.

Immediate for I, S and B types (each 12 bits) extended , immediate f for J type (20 bits).

Also in case of J and B , the immediates shifted to left by 3 bits (one bit is the discarded lsb in the machine code , other 2 bits to multiply the immediate by 4 because our memory is byte adresable)

It has two inputs (Data,ImmSel), ImmSel is 2-bit selector to select the suitable extended immediate for each type.

2.3.1 ImmGen Testing

| | | | |
|--|--|--|--|
| Test case 1: Data<= 32'hffffff. ImmSel <= 2'b00. Expected output is 32'h0000ffff | Test case 2 Data <= 32'h0000ffff. ImmSel <= 2'b01. Expected output is 32'hffffff | Test case 3 Data <= 32'hffffff. ImmSel <= 2'b10. Expected output is 32'h03ffffff | Test case 4 Data <= 32'h03ffffff. ImmSel <= 2'b11. Expected output is 32'hffffff |
|--|--|--|--|



2.4 Memory

This memory is byte-addressable, big Indian scheme which contain 64-location (256 byte), it writes on posedge of the clock, while the enable is activated if **MemWrt** is 1, then it is a write, otherwise it's a read.

The first 32-word (128 byte) are reserved for the instructions and the other 32-words are for data .

For more realistic memory it has **busy** signal which indicates weather mamory still operating or not , to hold the processor from doing anything during access memory time.

The bus is here bidirectional wire (inout) controlled by tri-state buffer using the enable signal **enMem** and write signal **MemWrt**, if both are enabled the data is reading from the memory, else it will be **Z** to be overwritten.

| Componen Description t | |
|---------------------------|--|
| Memory | 256-byte location for ROM and RAM (Can be extended) |
| Address Input | 32-bit address (addr), determines which location is to be read or written to |
| Data Port | Bidirectional, 32-bit |
| Control Signals | MemWrt : Determines read/write operation (1 for write, 0 for read) enMem : General enable control, If enMem is 1, then the register reads or writes depending on MemWrt . If enMem is 0, then nothing is done |
| Read Operation | Asynchronous |
| Write Operation | On positive edge of clock |
| Tri-state Buffer | 2 Tri-state Buffers, in case of reading from memory the write buffer puts the port on z state to allow the reading buffer putting data on the port, in case of writing on memory, the reading buffer puts the port on z state allowing the writing buffer to put data on the port |


2.4.1 Memory Testing

For memory testing we made the memory 32-byte location, and this is the testing criteria:


1. Writing on all locations with location address.
2. Reading from all locations (backward).
3. Try to write zero on all locations while enable is deactivated.
4. Write zero on all registers.

And by checking each location value after writing or checking the output after reading and the busy signal if the enable is 1 then it is activated, for each testcase notice the input signal which indicates write or reading.

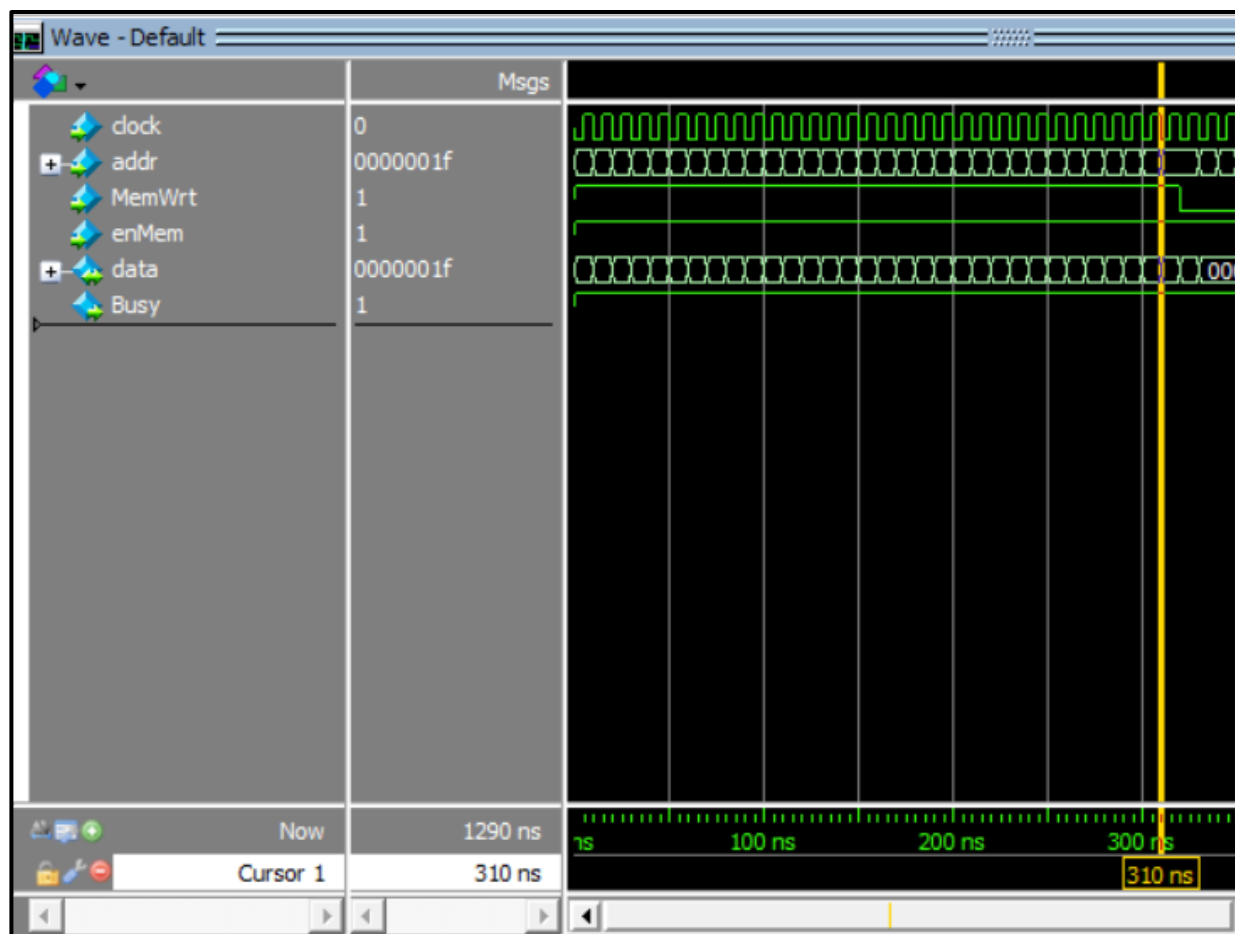
1. Writing on all locations with location address, $MemWrt, enMem = (1,1)$.



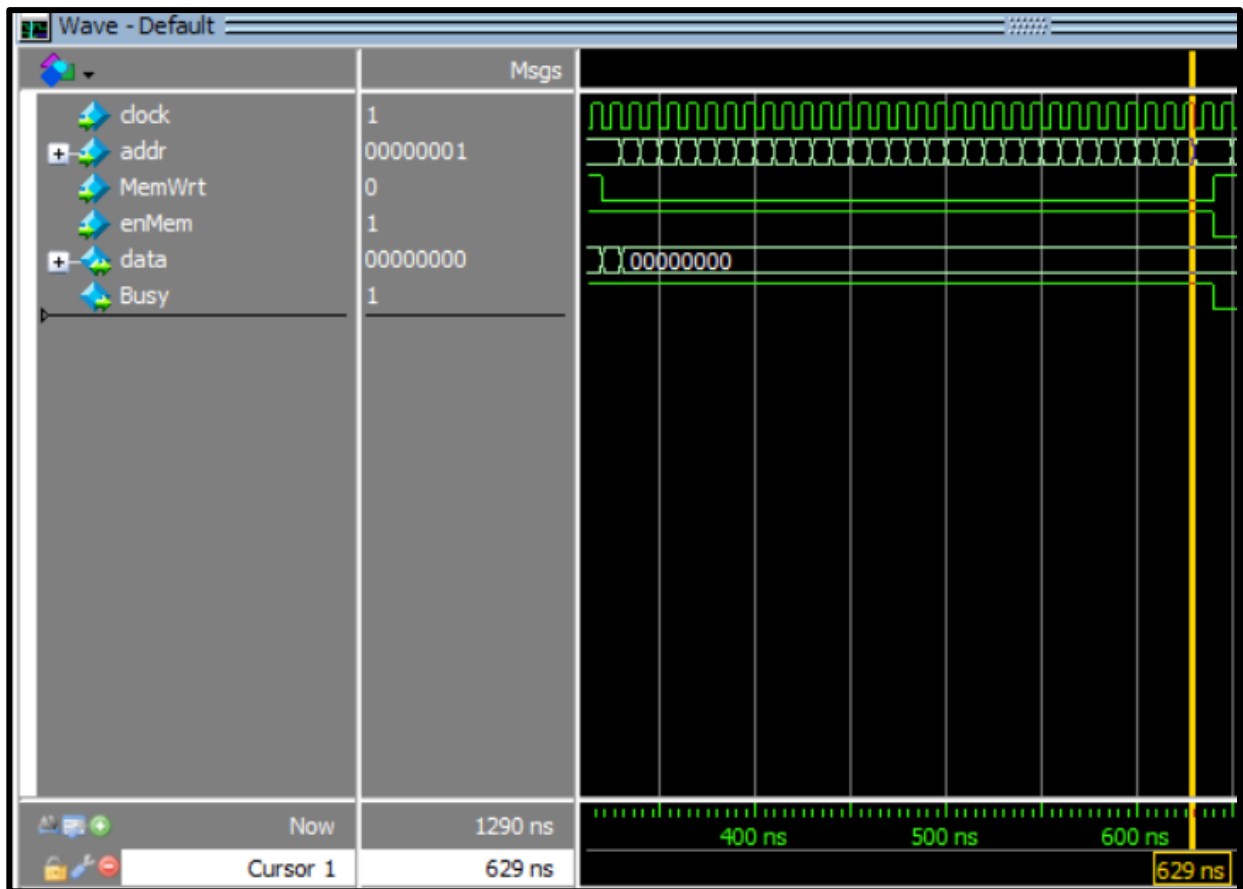
2. Reading from all locations (backward), $MemWrt, enMem = (0,1)$.



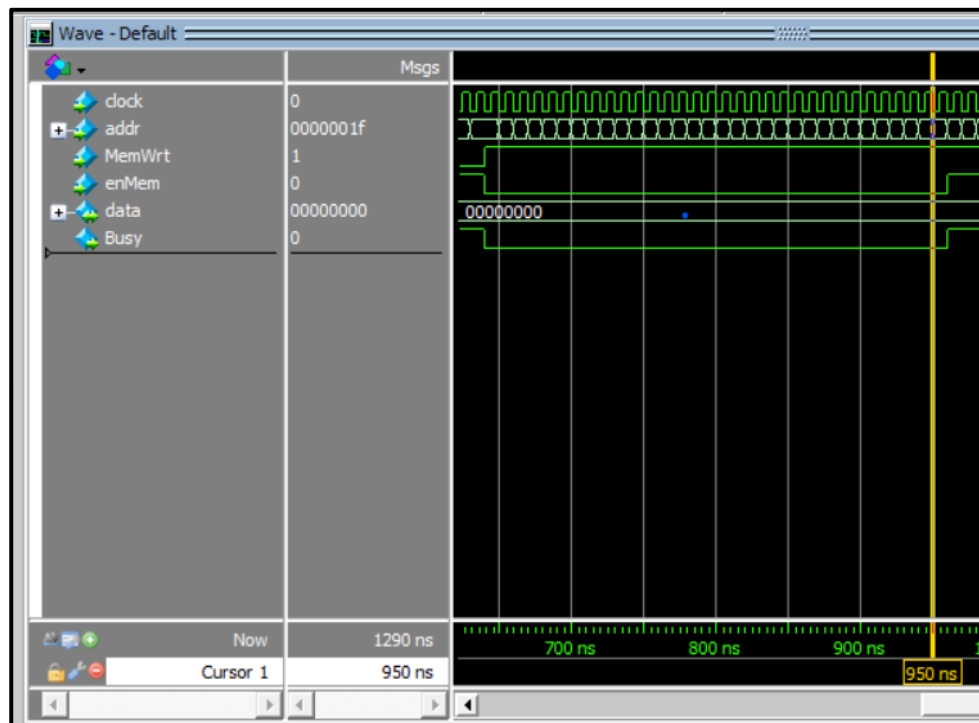3. Try to write zero on all locations while enable is deactivated
MemWrt, *enMem* = (1,0), note the data is forced at zero



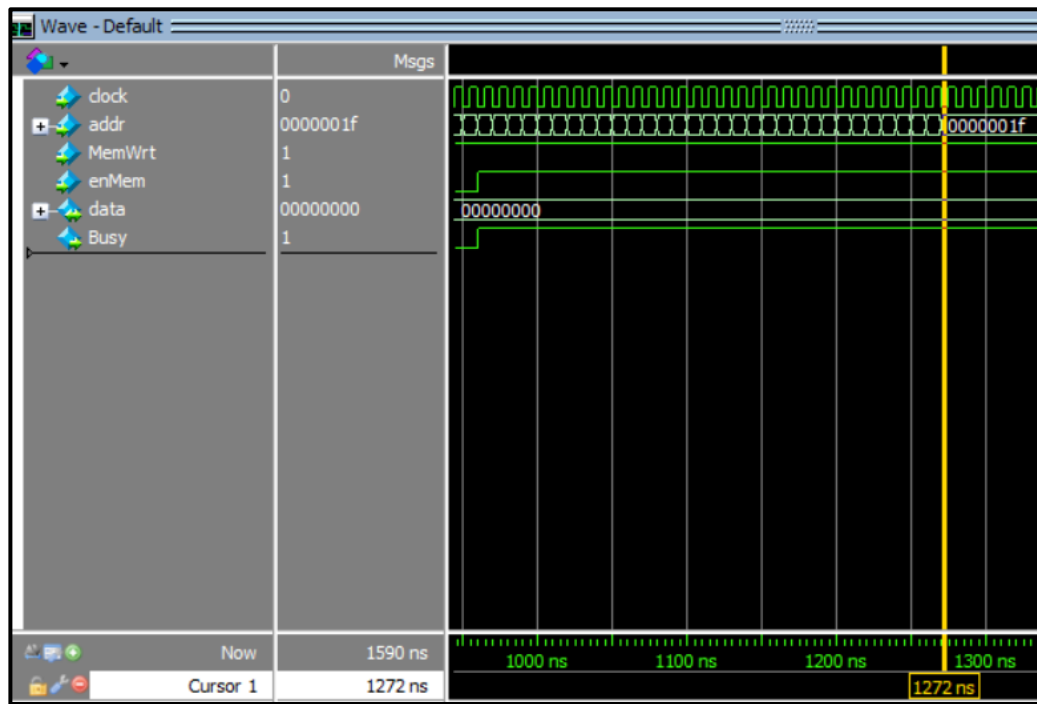
4. Write zero on all registers, deactivated *MemWrt*, *enMem* = (1,1).



3. Data path

a bus-based implementation of the RISC-V architecture. In this architecture, the different components of the machine share a common 32-bit bus through which they communicate. Control signals determine how each of these components is used and which components get to use the bus during a particular clock cycle.

Schematic Design:

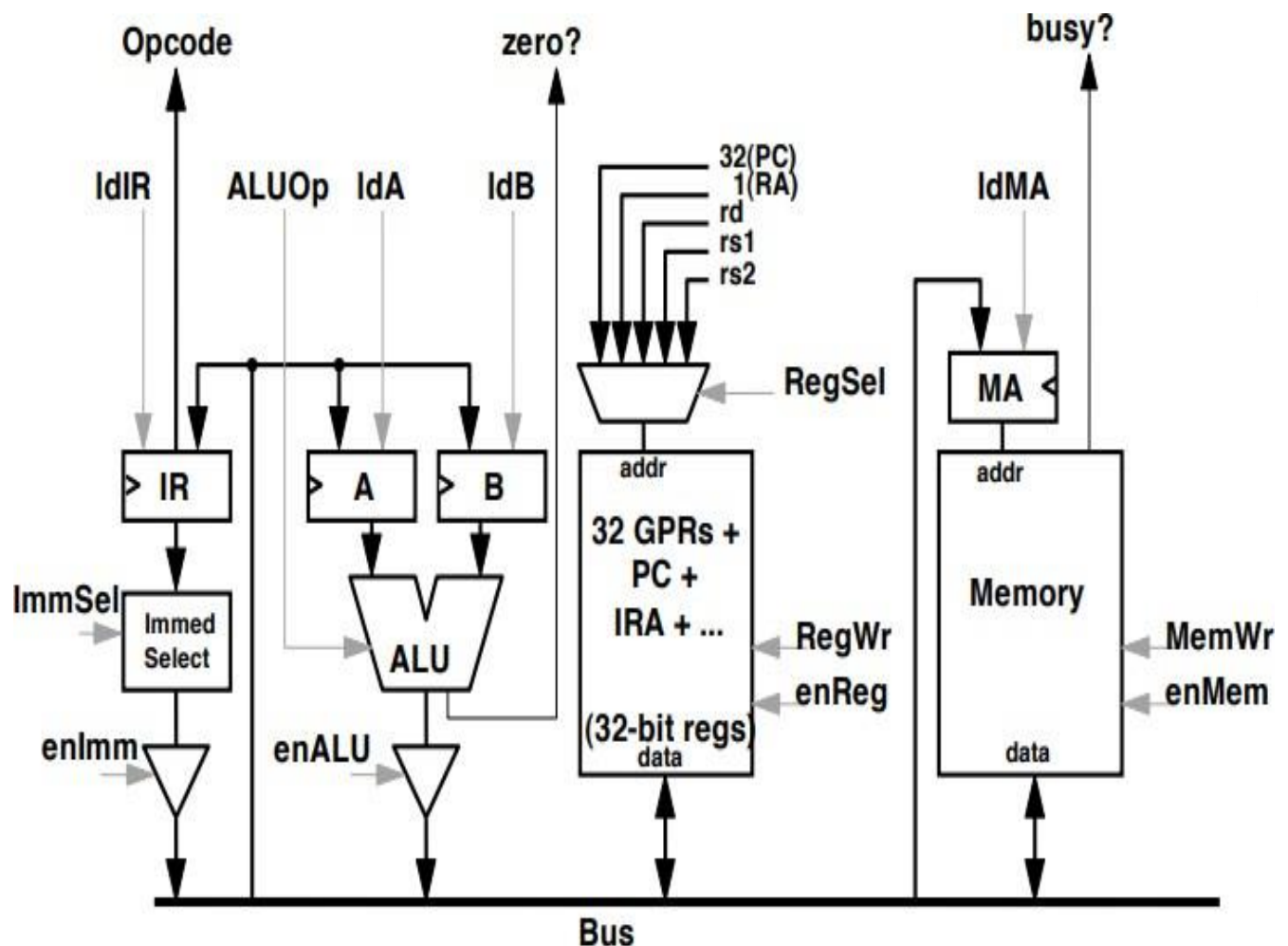

Supported instructions and their microcodes:

1) ADD instructions:

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|-----|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| DISPATCH | | | | | | | | | | | | | | | | |
| ADD0 | A -> REG[RS] | 0 | RS | 0 | 1 | 1 | X | X | 0 | X | X | 0 | X | 0 | N | X |
| ADD1 | B -> REG[RT] | 0 | RT | 0 | 1 | 0 | 1 | X | 0 | X | X | 0 | X | 0 | N | X |
| ADD2 | REG[RD] -> A+B | 0 | RD | 1 | 1 | 0 | 0 | ADD | 1 | X | X | 0 | X | 0 | J | FETCH |

2) SUB instruction:

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|-----|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| DISPATCH | | | | | | | | | | | | | | | | |
| SUB0 | A -> REG[RS] | 0 | RS | 0 | 1 | 1 | X | X | 0 | X | X | 0 | X | 0 | N | X |
| SUB1 | B -> REG[RT] | 0 | RT | 0 | 1 | 0 | 1 | X | 0 | X | X | 0 | X | 0 | N | X |
| SUB2 | REG[RD] -> A+B | 0 | RD | 1 | 1 | 0 | 0 | SUB | 1 | X | X | 0 | X | 0 | J | FETCH |

3) ADDI instruction:

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|-----|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| DISPATCH | | | | | | | | | | | | | | | | |
| ADDI3 | A -> REG[RS] | 0 | rs | 0 | 1 | 1 | x | x | 0 | x | x | 0 | x | 0 | N | X |
| ADDI4 | B -> imm | 0 | x | x | 0 | 0 | 1 | x | 0 | x | x | 0 | imm_1 | 1 | N | X |
| ADDI5 | REG[RD] -> A+B | 0 | rd | 1 | 1 | 0 | 0 | ADD | 1 | 0 | x | 0 | x | 0 | N | X |
| ADDI6 | | 0 | X | X | 0 | X | X | X | 0 | X | X | 0 | X | 0 | J | FETCH0 |

4) LW instruction:

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|-----|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| DISPATCH | | | | | | | | | | | | | | | | |
| LW0 | A -> OFFSET | 0 | X | X | 0 | 1 | X | X | 0 | X | X | 0 | SE16 | 1 | N | X |
| LW1 | B -> REG[RS] | 0 | RS | 0 | 1 | 0 | 1 | X | 0 | X | X | 0 | X | 0 | N | X |
| LW2 | MA -> A+B | 0 | X | X | 0 | 0 | 0 | ADD | 1 | 1 | X | 0 | X | 0 | N | X |
| LW3 | REG[RT] -> MEM | 0 | RT | 1 | 1 | X | X | X | 0 | 0 | 0 | 1 | X | 0 | S | |
| LW4 | | 0 | X | X | 0 | X | X | X | 0 | X | X | 0 | X | 0 | J | FETCH0 |

5) SW instruction

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|-----|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| DISPATCH | | | | | | | | | | | | | | | | |
| SW0 | A -> OFFSET | 0 | X | X | 0 | 1 | X | X | 0 | X | X | 0 | SE16 | 1 | N | X |
| SW1 | B -> REG[RS] | 0 | RS | 0 | 1 | 0 | 1 | X | 0 | X | X | 0 | X | 0 | N | X |
| SW2 | MA -> A+B | 0 | X | X | 0 | 0 | 0 | ADD | 1 | 1 | X | 0 | X | 0 | N | X |
| SW3 | MEM -> REG[RT] | 0 | RT | 0 | 1 | X | X | X | 0 | 0 | 1 | 1 | X | 0 | S | |
| SW4 | | 0 | X | X | 0 | X | X | X | 0 | X | X | 0 | X | 0 | J | FETCH0 |

6) Jump instruction:

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|-----|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| DISPATCH | | | | | | | | | | | | | | | | |
| J0 | B -> immJ | 0 | X | X | 0 | 1 | 1 | X | 0 | X | X | 0 | imm_j | 1 | N | X |
| J1 | PC -> A + B | 0 | pc | 1 | 1 | 0 | 0 | ADD | 1 | X | X | 0 | X | 0 | N | X |
| J3 | | 0 | X | X | 0 | X | X | X | 0 | X | X | 0 | X | 0 | J | FETCH0 |

7) BEQ instruction:

| State | PseudoCode | ld IR | RegSel | RegW | enReg | ld A | ld B | ALUOp | enALU | ldMA | MemW | enMem | EXSel | enImm | MBr | Nest State |
|----------|-----------------|-------|--------|------|-------|------|------|---------|-------|------|------|-------|-------|-------|------|------------|
| FETCH0 | MA -> PC | 0 | PC | 0 | 1 | 1 | X | X | 0 | 1 | X | 0 | X | 0 | N | X |
| | A -> PC | | | | | | | | | | | | | | | |
| FETCH1 | IR -> MEM[MA] | 1 | X | X | 0 | 0 | X | X | 0 | 0 | 0 | 1 | X | 0 | S | X |
| FETCH2 | PC -> PC(A) + 4 | 0 | PC | 1 | 1 | 0 | X | INC_A_4 | 1 | X | X | 0 | X | 0 | D | X |
| | | | | | | | | | | | | | | | | |
| DISPATCH | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | | |
| BEQ0 | A -> REG[RS] | 0 | RS | 0 | 1 | 1 | X | X | 0 | X | X | 0 | X | 0 | N | X |
| BEQ1 | B -> REG[RT] | 0 | RT | 0 | 1 | 0 | 1 | X | 0 | X | X | 0 | X | 0 | N | X |
| BEQ2 | A -> A-B | 0 | X | X | 0 | 1 | 0 | SUB | 1 | X | X | 0 | X | 0 | FNEZ | FETCH0 |
| BEQ3 | A -> REG[PC] | 0 | PC | 0 | 1 | 1 | 0 | X | 0 | X | X | 0 | X | 0 | N | X |
| BEQ4 | B -> imm | 0 | X | X | 0 | 0 | 1 | X | 0 | X | X | 0 | imm_B | 1 | N | X |
| BEQ5 | REG[PC] -> A+B | 0 | pc | 1 | 1 | 0 | 0 | ADD | 1 | x | x | 0 | x | 0 | N | x |
| | | 0 | X | X | 0 | X | X | X | 0 | X | X | 0 | X | 0 | J | FETCH0 |

Datapath testing

In order to test each instruction without control unit , we have to pass inputs control signals manually to the data path in the test bench .

First initialize data memory with instructions and data


Machine codes found in “Memory_init.txt” also

| | | |
|----------|-------------|-------------------|
| Word0: | 00 A0 02 93 | //ADDI X5,X0,10 |
| Word1: | 00 50 03 B3 | //ADD X7,X5,X0 |
| Word2: | 40 72 82 B3 | //SUB X5,X5,X7 |
| Word3: | 08 00 24 03 | //LW X8,128(X0) |
| Word4: | 08 80 22 23 | // SW X8, 132(X0) |
| Word5: | 00 40 00 6F | //J 4 |
| Word6: | 00 00 00 00 | |
| Word7: | 00 00 00 00 | |
| Word8: | 00 00 00 00 | |
| Word9: | 00 A0 02 93 | // ADDI X5,X0,10 |
| Word10 : | 00 72 82 63 | // BEQ x5,x7,5 |
| Word11: | 01 40 02 93 | //ADDI X5,X0,20 |
| Word12: | 00 00 00 00 | |
| Word13: | 00 00 00 00 | |
| Word14: | 00 00 00 00 | |
| Word15: | 40 72 82 B3 | //SUB X5,X5,X7 |
| | | |
| Word32: | 11 00 11 FF | //Data |

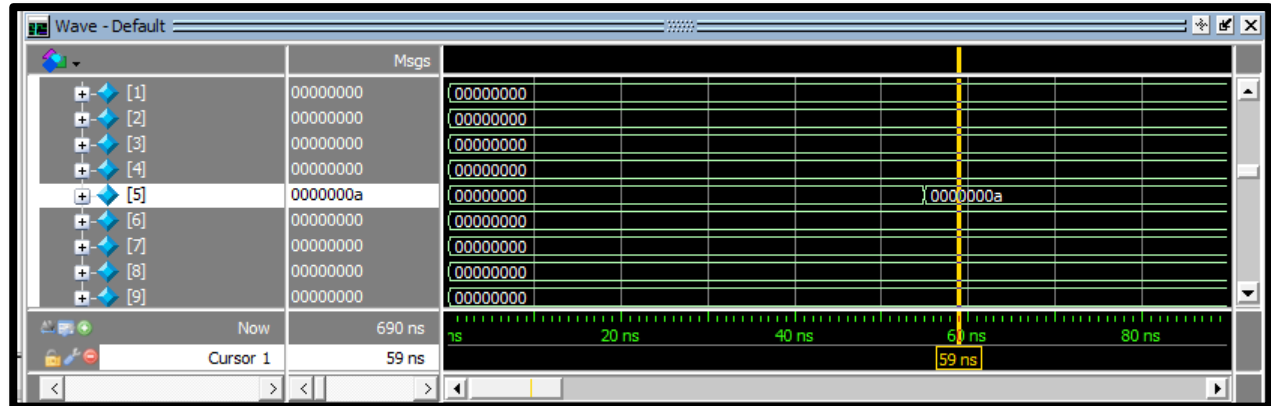1) Final Results after executing first instruction:

ADDI X5,X0,10


Expected to write value of 10 on register x5



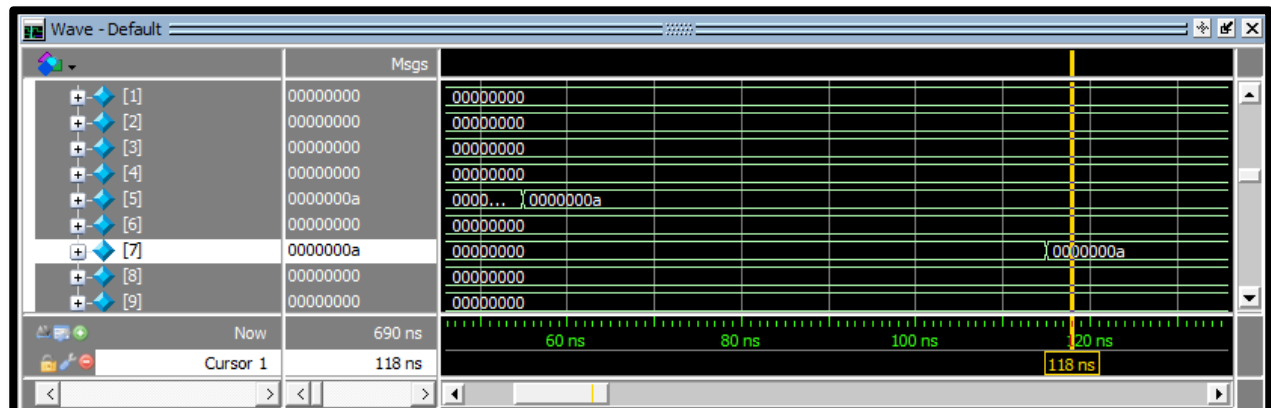2) Executing second instruction :

ADD X7,X5,X0


Expected to copy value of register x5 to register x7 which is 10



3) Executing third instruction:

SUB X5,X5,X7


Expected to clear register x5

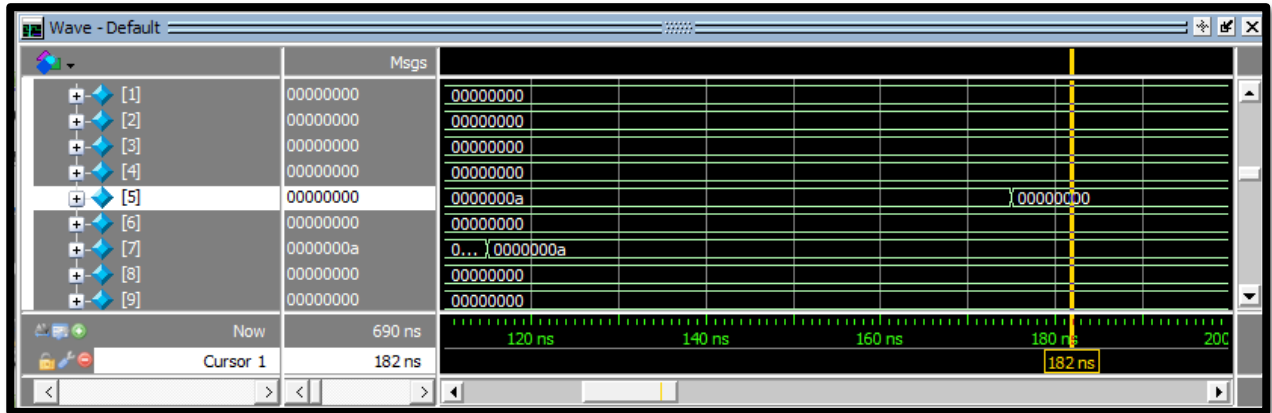

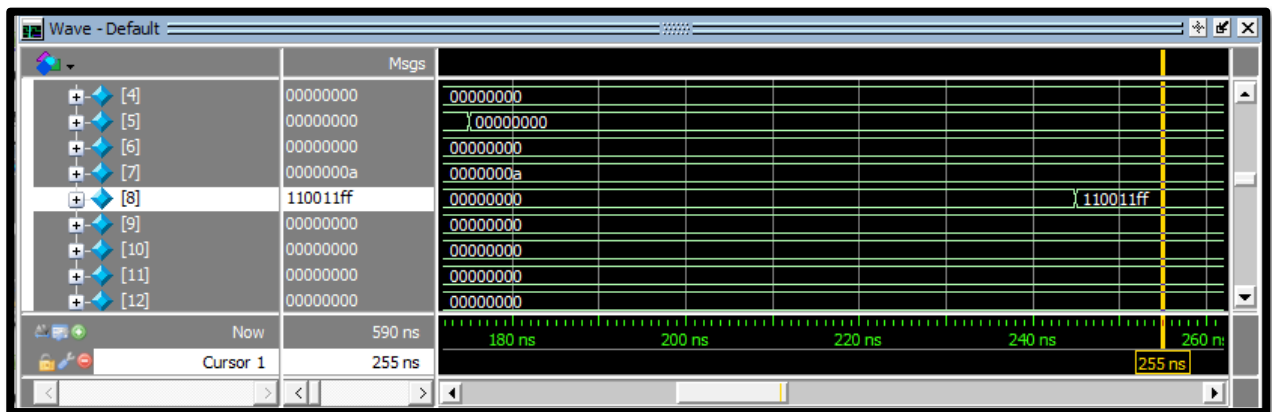4) Executing fourth instruction:

LW X8,128(X0)


Expected to load value (0x 11 00 11 ff) from memory into register x8 (0x 11 00 11 ff stored at word 32 in memory)



 5) Executing Fifth instructions:

SW X8, 132(X0)

Expected to store value of register X8(0x 11 00 11 ff) into word 33 of memory




| | |
|----------|-------------|
| 00000080 | 11 00 11 ff |
| 00000084 | 11 00 11 ff |

6) Executing sixth instruction:

J 0x4

Expected to jump to instruction at word 9 of memory


And fetching (ADDI X5,X0,10) instruction

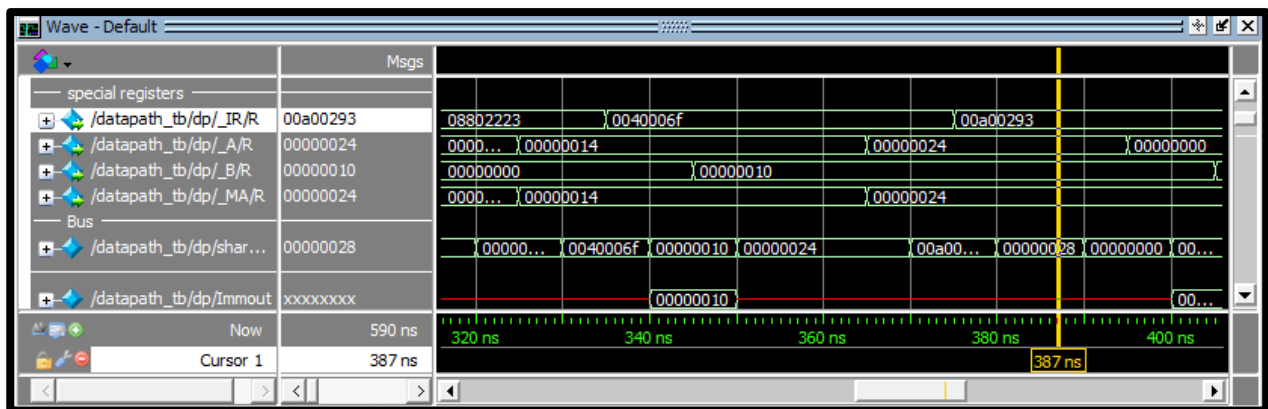

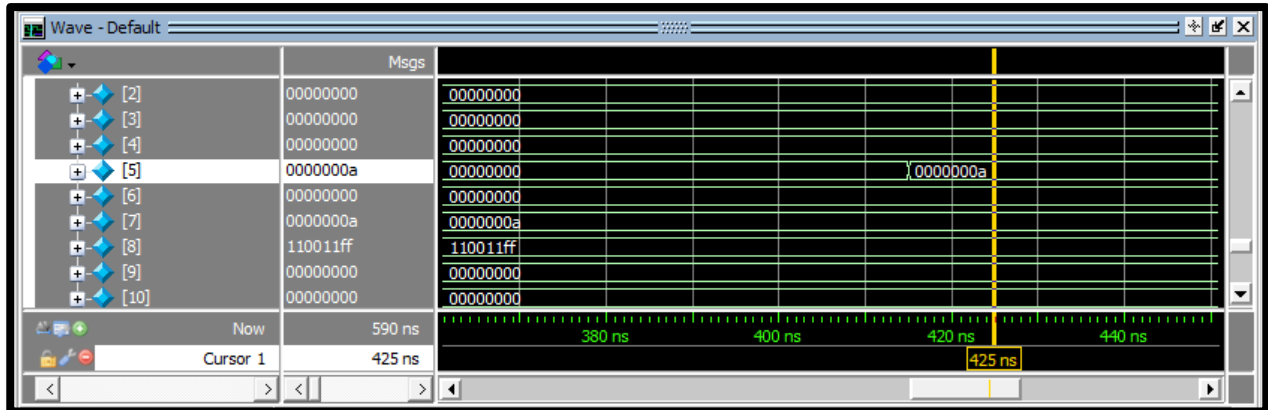7) Executing seventh instruction:

ADDI X5,X0,10


Expected to write value of 10 on register x5 again



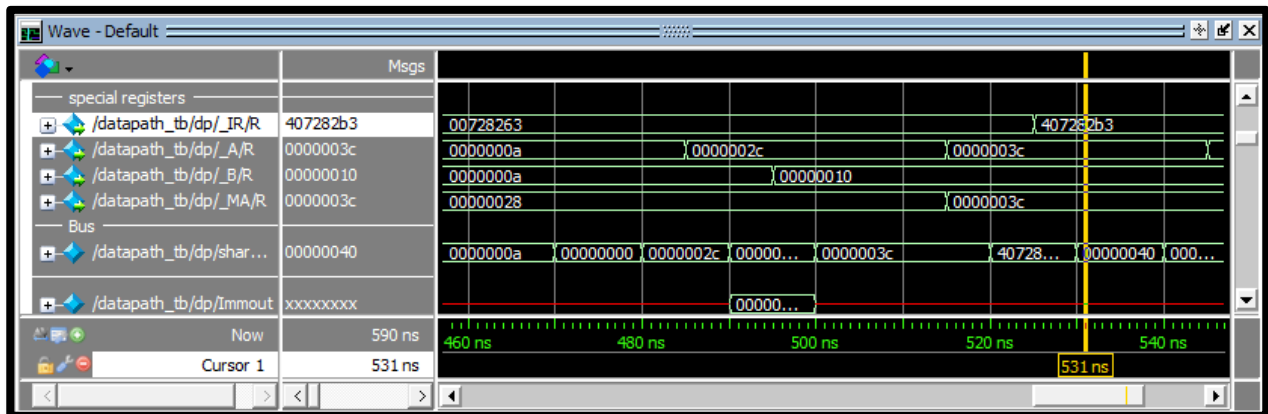8) Executing Eighth instruction

BEQ x5,x7,5


While X5 == X7 = > 10, Expected to jump to instruction in word 16 (SUB X5,X5,X7) instead of fetching next instruction (ADDI X5,X0,20)




9) Executing ninth and last instruction

SUB X5,X5,X7

Expected to clear register X5 again

 


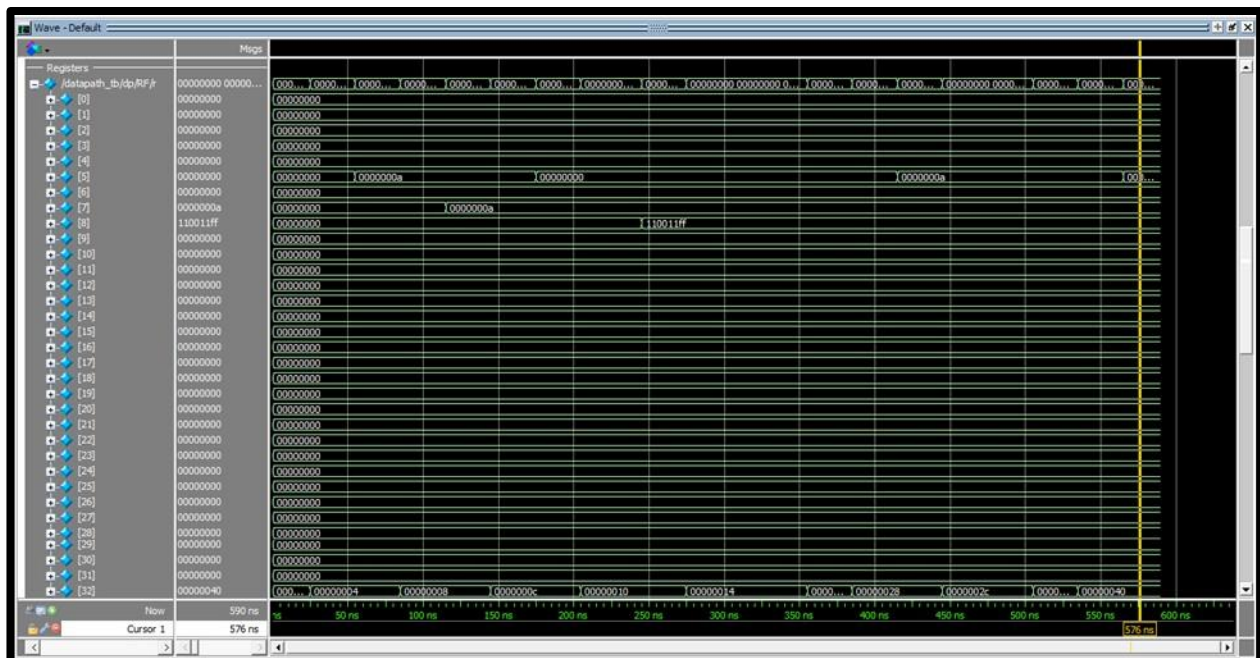- Final view of registers values in register file



General view of the waveforms:

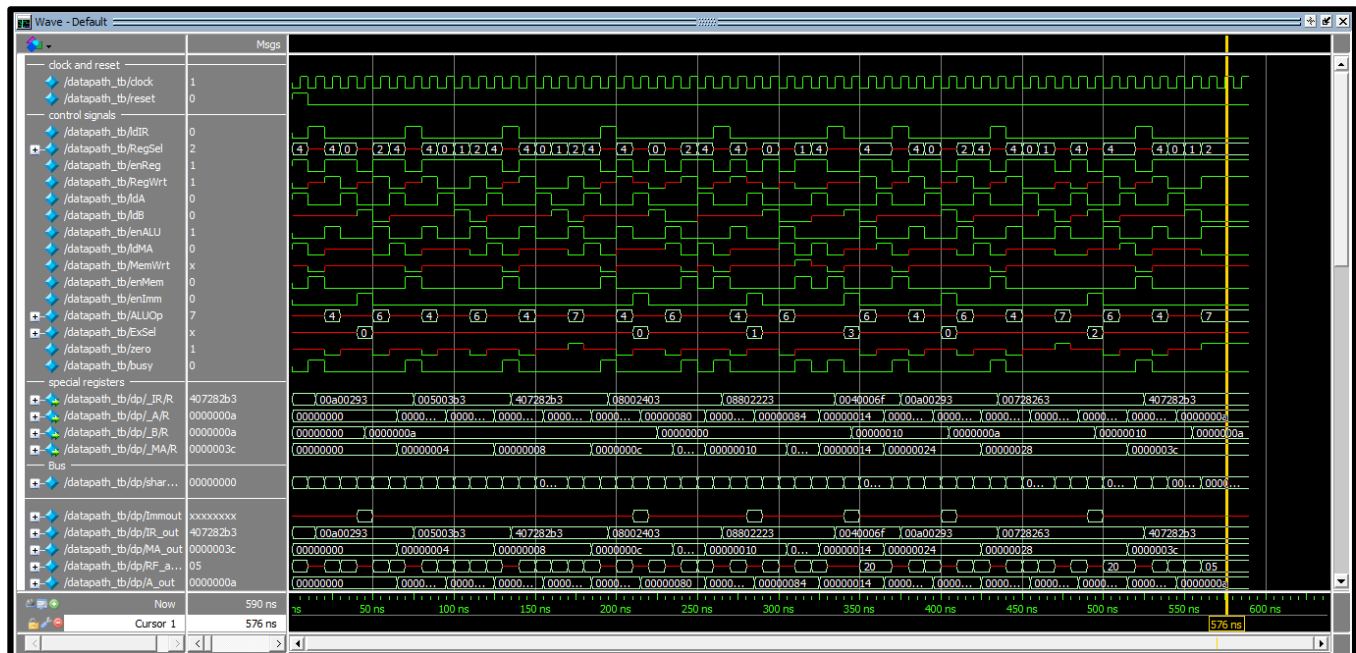Note : you can find .do file for the waveform signal (wave.do)



Micro coded Control Unit

ROM-based microcoded control unit

manages the CPU by storing micro-operations in a ROM, each representing a control signal sequence for executing specific instructions. The first three bits of each micro-operation indicate the next state, enabling the control unit to fetch subsequent micro-operations.

Micro-Operation Storage

The micro-operations are stored in a ROM, with each location containing a single microcode. The organization of the ROM is as follows:

- **Address 0:** Reset operation
- **Addresses 1 to 3:** Fetch microcodes
- **Address 4:** Dispatch operation
- **Addresses 5 to 7:** ADD instruction microcodes
- **Addresses 8 to 10:** SUB instruction microcodes
- **Addresses 11 to 13:** ADDI instruction microcodes
- **Addresses 14 to 17:** LW instruction microcodes
- **Addresses 18 to 21:** SW instruction microcodes
- **Addresses 22 to 27:** BEQ instruction microcodes
- **Addresses 28 to 30:** JAL instruction microcodes

Micro Program Counter (μ PC)

The μ PC determines the address of the micro-operation to fetch from the ROM. The μ PC is updated based on the **nextState** value, which is derived from the first three bits of the current micro-operation.


State Definitions

- **Fetch:** Initiates the fetch operation by setting the μ PC to 1.
- **Next:** Increments the μ PC to point to the next microcode.
- **Dispatch:** Uses the OP_GROUPS value to set the μ PC, determining the starting address of the microcodes for the current instruction.
- **FNEZ:** Checks if the zero flag is not set. If true, resets the μ PC; otherwise, increments it by 1.
- **FEQZ:** Checks if the zero flag is set. If true, increments the μ PC by 1; otherwise, resets it.

Dispatch Operation

The dispatch operation depends on the opcode and function fields of the current instruction. The value of OP_GROUPS is determined based on these fields and holds the starting address of the microcodes for the instruction to be executed.

 Observe the value of MPC how it move from micro code to another



Rest of instructions will be tested on the data path with control unit

Testing DataPath Again After implementing control unit:


testing same benchmark we tested earlier :

Machine codes found in "Memory_init.txt" also


| | | |
|----------|-------------|-------------------|
| Word0: | 00 A0 02 93 | //ADDI X5,X0,10 |
| Word1: | 00 50 03 B3 | //ADD X7,X5,X0 |
| Word2: | 40 72 82 B3 | //SUB X5,X5,X7 |
| Word3: | 08 00 24 03 | //LW X8,128(X0) |
| Word4: | 08 80 22 23 | // SW X8, 132(X0) |
| Word5: | 00 40 00 6F | //J 4 |
| Word6: | 00 00 00 00 | |
| Word7: | 00 00 00 00 | |
| Word8: | 00 00 00 00 | |
| Word9: | 00 A0 02 93 | // ADDI X5,X0,10 |
| Word10 : | 00 72 82 63 | // BEQ x5,x7,5 |
| Word11: | 01 40 02 93 | //ADDI X5,X0,20 |
| Word12: | 00 00 00 00 | |
| Word13: | 00 00 00 00 | |
| Word14: | 00 00 00 00 | |
| Word15: | 40 72 82 B3 | //SUB X5,X5,X7 |
| | | |
| Word32: | 11 00 11 FF | //Data |

General view of the waveforms:

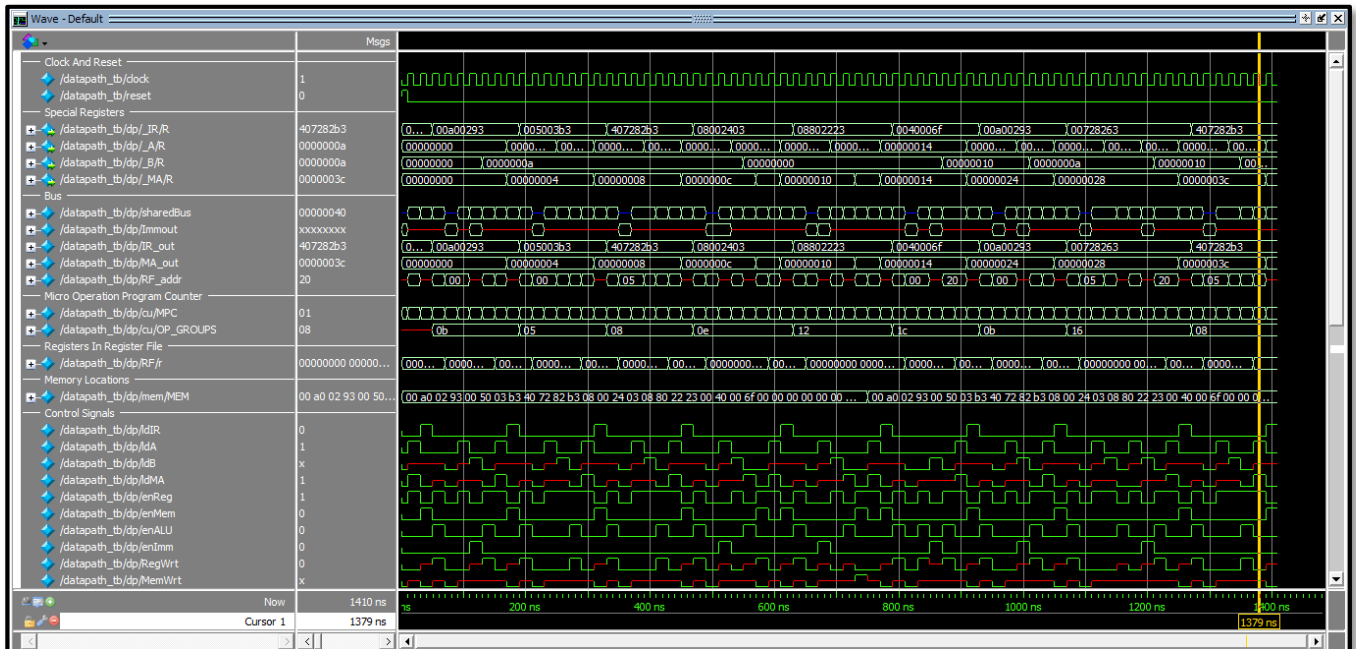
Note : you can find .do file for the waveform signal (wave.do)



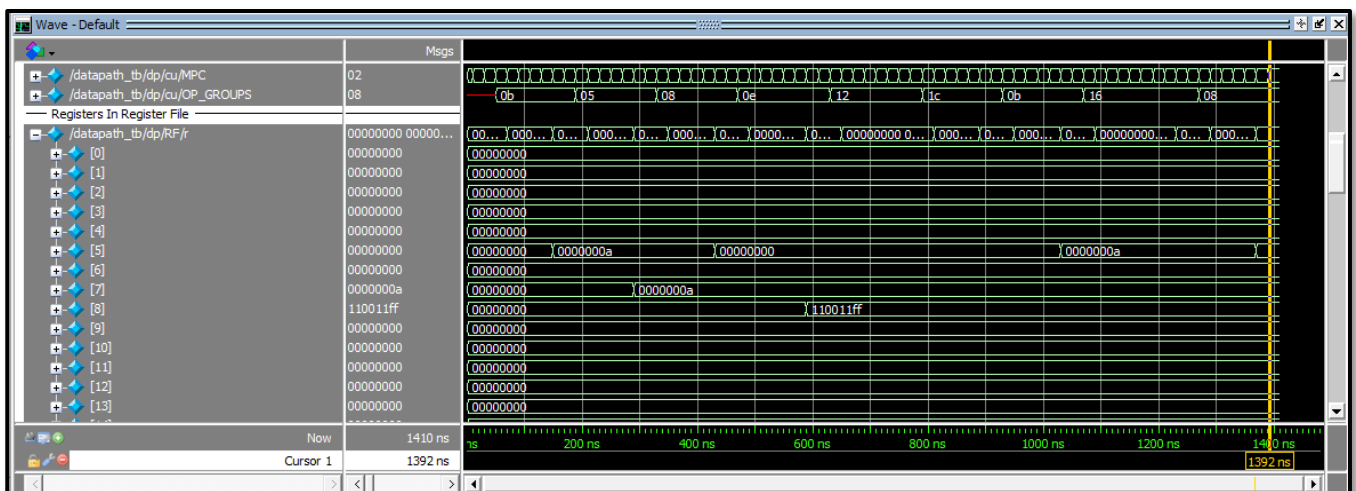- Final view of registers values in register file



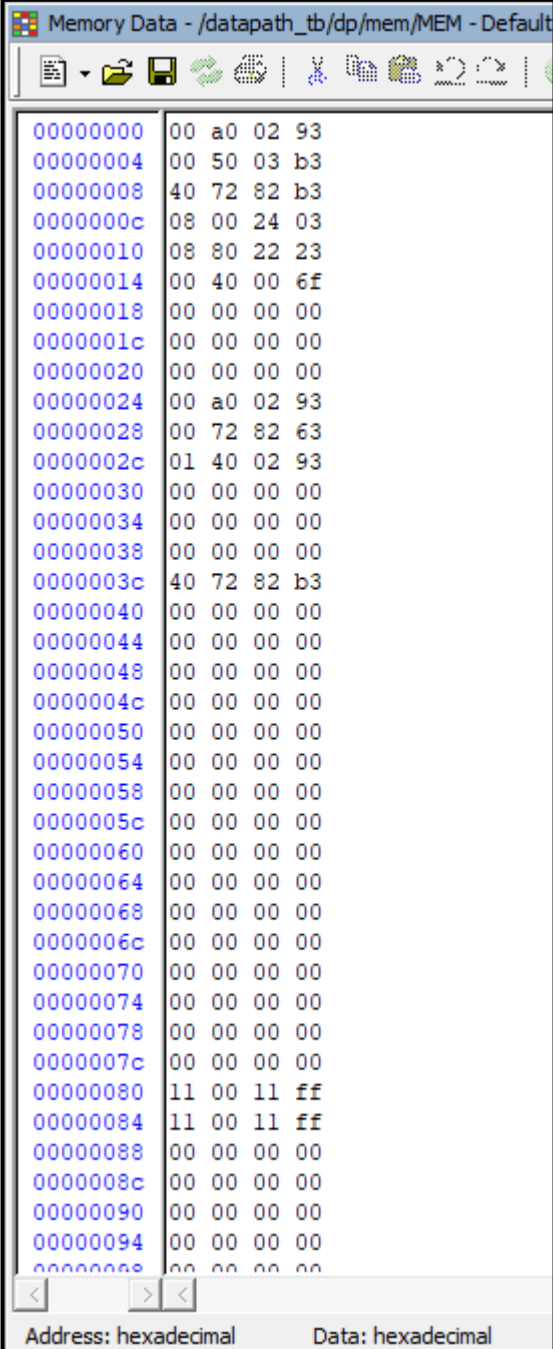- Final view of Memory values after executing the program



| | | | | |
|----------|----|----|----|----|
| 00000000 | 00 | a0 | 02 | 93 |
| 00000004 | 00 | 50 | 03 | b3 |
| 00000008 | 40 | 72 | 82 | b3 |
| 0000000c | 08 | 00 | 24 | 03 |
| 00000010 | 08 | 80 | 22 | 23 |
| 00000014 | 00 | 40 | 00 | 6f |
| 00000018 | 00 | 00 | 00 | 00 |
| 0000001c | 00 | 00 | 00 | 00 |
| 00000020 | 00 | 00 | 00 | 00 |
| 00000024 | 00 | a0 | 02 | 93 |
| 00000028 | 00 | 72 | 82 | 63 |
| 0000002c | 01 | 40 | 02 | 93 |
| 00000030 | 00 | 00 | 00 | 00 |
| 00000034 | 00 | 00 | 00 | 00 |
| 00000038 | 00 | 00 | 00 | 00 |
| 0000003c | 40 | 72 | 82 | b3 |
| 00000040 | 00 | 00 | 00 | 00 |
| 00000044 | 00 | 00 | 00 | 00 |
| 00000048 | 00 | 00 | 00 | 00 |
| 0000004c | 00 | 00 | 00 | 00 |
| 00000050 | 00 | 00 | 00 | 00 |
| 00000054 | 00 | 00 | 00 | 00 |
| 00000058 | 00 | 00 | 00 | 00 |
| 0000005c | 00 | 00 | 00 | 00 |
| 00000060 | 00 | 00 | 00 | 00 |
| 00000064 | 00 | 00 | 00 | 00 |
| 00000068 | 00 | 00 | 00 | 00 |
| 0000006c | 00 | 00 | 00 | 00 |
| 00000070 | 00 | 00 | 00 | 00 |
| 00000074 | 00 | 00 | 00 | 00 |
| 00000078 | 00 | 00 | 00 | 00 |
| 0000007c | 00 | 00 | 00 | 00 |
| 00000080 | 11 | 00 | 11 | ff |
| 00000084 | 11 | 00 | 11 | ff |
| 00000088 | 00 | 00 | 00 | 00 |
| 0000008c | 00 | 00 | 00 | 00 |
| 00000090 | 00 | 00 | 00 | 00 |
| 00000094 | 00 | 00 | 00 | 00 |
| 00000098 | 00 | 00 | 00 | 00 |

Address: hexadecimal Data: hexadecimal